

Transformation of energy

Teachers Notes - Lesson 3 - Slide 16

Quiz: Ask your students to identify which circuits will make the light bulb glow.

Which of these electrical circuits will make the light bulb glow?

Correct answers: A & C

Class discussion:

- Ask some students to present their observations to the class.
- What circuits made the light bulb glow?
- What did the circuits that made the light bulb glow have in common?
- What did the circuits that didn't work have in common?

(Introduce the terms open and closed circuits)